
ELE863/EE8501 VLSI Systems

Simultaneous Switching Noise (SSN)

 

Fei Yuan, Ph.D, P.Eng.
Professor and Ryerson Research Chair
Department of Electrical and Computer Engineering
Ryerson University
Toronto, Ontario, Canada
Copyright © Fei Yuan, 2009

Preface

 $\,\vartriangleright\,$ This chapter deals with simultaneous switching noise (SSN). The reduction of SSN is critical for mixed-mode circuits. In this chapter, we investigate the sources of SSN and the effect of SSN. Techniques that reduce the effect of SSN are examined in detail. The design criteria for SSN are studied. The grounding schemes of analog and digital circuits are investigated.

OUTLINE

- Simultaneous Switching Noise (SSN)
- Effect of SSN
- Analysis of SSN
- SSN Reduction Techniques
- Design Criteria for SSN
- Analog and Digital Grounding

SSN

 


Figure 1: Bonding wires, bonding pads, traces, and pins.

- ▶ Bonding wires, bonding pads, traces, and pins form the interface path between circuits on the chip and circuits on boards.
- ▶ The resistance, capacitance, and inductance of the interface paths largely determine the performance of systems.

 


Figure 2: Bonding wires, bonding pads, traces, and pins.

- ▶ Bonding wires at the corners are the longest These wires have the largest resistance and inductance.
- ▶ The use of the bonding pads at the corners and the bonding wires connected to these pads should be avoided.
- ▶ The design rules of most CMOS technologies typically prohibit the use of the bonding pads at the corners. These pads should be used as "dummy", i.e. no electrical connections to these pads.

 


Figure 3: Bond pads and bond wires.

• Bond Pads

- \triangleright Bond pads are on-chip metal rectangles large enough to be soldered to leads, typically 70x70 μm^2 100x100 μm^2 .
- ▶ Each pad is typically formed by the two top-most metal layers connected to each other by many vias on the perimeter in order to avoid the *lift-off* of the top metal layer during bonding.
- Some CMOS processes require that all metal layers to be connected together for bond pads. Because the top metal layer has a smaller capacitance to the substrate as compared with the bottom metal layer, connecting all bond-pad metal layers together will dramatically increase the capacitance of the pad to the substrate.
- ▶ Do not lay pads at the corners of the chip. Add dummy pads at the corners instead.

▶ The capacitance of bond pads consists of two components : (i) the area capacitance and (ii) the fringe capacitance

$$C_{Pad} \approx \epsilon_{ox} \left[1.15 \frac{A}{H} + 2.8 \left(\frac{T}{H} \right)^{0.222} P \right], \tag{1}$$

where A=pad area, P=pad periphery, H=height of pad above conductive silicon substrate, T=thickness of pad, ϵ_{ox} =dielectric constant of silicon dioxide. The first term gives the area capacitance whereas the second term quantifies the fringe capacitance (Ref. T. Sakurai and K. Tamaru, "Simple formulas for two- and three-dimensional capacitances," *IEEE Trans. Electron Devices*, Vol.30, No. 2, pp.183-185, Feb. 1983.)

 \triangleright H increases $\longrightarrow C_{pad}$ decreases. For high-speed applications, only the top metal layers, such as top two metal layers, should be used for signal pads. For V_{DD} and V_{DD} pads, all metal layers can be connected together to form pads.

 


Figure 4: Bonding pads are formed by topmost metal layers.

 \triangleright Typically $C_{pad} = 0.2 - 0.4$ pF for a $100 \times 100 \mu m$ pad.

• Inductance of Package

▷ Self-Inductance:

$$L_{ij} = \frac{\psi_{ij}}{I_j} = \frac{\int \int \mathbf{B}_{ij} \bullet d\mathbf{s}_{ij}}{I_j}, \qquad (2)$$

 ψ_{ij} and \mathbf{B}_{ij} are the flux and intensity of the magnetic field that is generated by I_j and passes through loop i. L_{jj} , is called the self-inductance quantifying the relation between the magnetic flux of loop j and the current of loop j, L_{ij} , $i\neq j$ is called mutual inductance.

 


Figure 5: Self-inductance definition.

• Inductance of Package (cont'd)

▷ Self inductance of a round bond wire

 


Figure 6: Self-inductance of a round wire.

$$L \approx \frac{\mu_o l}{2\pi} \left[\ln \left(\frac{2H}{R} \right) - 0.75 \right],$$
 (3)

where L=inductance per unit length, R=radius of the conductor, H distance from the conductive substrate, and μ_o =permittivity of free space. Typically, $L\approx1$ nH/mm for bond wires. (Ref. T. Lee, *The Design of COS Radio-Frequency Integrated Circuits*, 2nd ed., Cambridge University Press, 2004).

 \triangleright Self-Inductance of a rectangular trace

 


Figure 7: Self-inductance of a rectangular trace.



where L= inductance per unit length, $K_f \approx 0.72(\frac{H}{W}) + 1$ (fringe factor), W=width of the trace and H=distance from the trace to the conductive substrate.

▶ Mutual Inductance of two round wires of equal length

 


Figure 8: Mutual-inductance definition.

 


Figure 9: Mutual-inductance of two round wires.

 \triangleright

$$M = \frac{\mu_o l}{2\pi} \left[\ln \left(\frac{2l}{d} \right) - 1 + \frac{d}{l} \right],\tag{5}$$

where L=inductance per unit length, l=length of bond wires, d=distance between bond wires

⊳ For 10-mm length and 1-mm spacing, $M\approx4$ nH. Since $L\approx10$ nH, the coupling coefficient is 40% approximately.

• The Max. Frequency of Interfaces

▶ The capacitance of band pads and the inductance of bond wires form a 2nd-order low-pass. The upper limit of I/O frequency is set by the cutoff frequency of the low-pass. From

$$H(s) = \frac{V_o(s)}{V_{in}(s)} = \frac{1}{s^2 L_{wire} C_{total} + 1},$$
 (6)

where V_{in} and V_o are the voltage at the pin and the pad of the interface, respectively, we have

$$\omega_{-6dB} = \frac{1}{\sqrt{L_{wire}C_{total}}},\tag{7}$$

where $C_{total} = C_{pad} + C_{pkg}$.

▶ When choosing packages, the highest design frequency of your design must not exceed the cutoff frequency of the I/O package.

• Lumped Model of Bond Wires

 


Figure 10: Lumped model of bond wires.

- \triangleright R_{ss} =series resistance of bonding wires, L_{ss} =self and mutual inductances of bonding wires, C_{ss} =package capacitance.
- \triangleright Bond wires are mainly inductive at high frequencies. Typical $L_{ss} \ge 5 \,\mathrm{nH}$, and are usually modeled as an inductor.
- \triangleright If a high-frequency current flows through a bonding wire, a voltage drop across the bonding wire quantified by $V_L(t) = L_{ss} \frac{di(t)}{dt}$ is generated.
- \triangleright This voltage drop affects on-chip V_{DD} and V_{ss} for V_{DD} and V_{ss} pads and on-chip signals for signal pads.

• Output Buffers

 


Figure 11: On-chip V_{DD} & V_{ss} fluctuate due to switching noise.

- ▶ Load capacitance of the inverter includes (1) Output capacitance of output buffer, (2) Capacitance of bond pads, (3) Capacitance of package, and (4) Capacitance of off-chip printed-circuit-board (PCB) traces.
- ▷ Off-chip capacitances are typically much larger than on-chip capacitances.
- ▶ To meet timing constraints, large output buffers (wide inverters) are needed to drive off-chip capacitive loads.

$$W/L\uparrow \longrightarrow R_{on}\downarrow \longrightarrow \tau\downarrow.$$

$$W/L\uparrow \longrightarrow C_{out}\uparrow \longrightarrow C_L\uparrow.$$

• Output Buffers (cont'd)

- \triangleright The load capacitance is typically $1 \sim 30$ pF. Typical size of output buffers $500 \sim 1000 \mu m$.
- ▶ The size of inverter should be increased by a factor of e = 2.71828. The optimal number of inverters is such that the input capacitance of the last inverter should be 1/e that of the load capacitance (Ref. C. Mead and L. Conway, *Introduction to VLSI systems*, Addison-Wesley, 1980).
- \triangleright Typical ratio of 4 \sim 5 is used in sizing output buffers in order to save silicon area.
- ▶ Static inverter-based output buffers can be used for clock speed up to a few hundred MHz. These output buffers can not be used for very high-speed clock speeds.

• Charging/discharging Currents of Output Buffers

- ▶ Large charging/discharging current spikes
 - 1) C_L is large, because $i_C(t) = C_L \frac{v_C(t)}{dt} \longrightarrow i_C(t)$ is large.
 - 2) Sharp rising/falling edges $\longrightarrow \frac{v_C(t)}{dt}$ is large $\longrightarrow i_C(t)$ is large.

 


Figure 12: Large charging/discharging current spikes and the fluctuation of on-chip V_{DD} and V_{ss} .

• Switching Noise

 


Figure 13: Noisy on-chip $V_{DD} \& V_{ss}$.

- \triangleright When sharp charging/discharging currents of output buffers flow through the bond wires of V_{DD} and V_{ss} , large voltage drops $v_{L,DD}$ and $v_{L,ss}$ across the bond wires are generated
- \triangleright On-chip V_{DD} and V_{ss} vary with switching \longrightarrow power fluctuation and ground bouncing:

$$v_{DD,on-chip} = V_{DD} - v_{L,DD}$$

$$v_{SS,on-chip} = V_{ss} - v_{L,ss}$$
 (8)

• Simultaneous Switching Noise (SSN)

 


Figure 14: Simultaneous switching noise.

 ► Large switching noise at power and ground rails exist if multiple buffers switch simultaneously — Simultaneous switching noise (the Worst Case).

$$V_{DD,on-chip} = V_{DD} - v_{L,DD},$$

$$v_{L,DD} = L_{DD} \frac{i_{DD}}{dt} = L_{DD} \sum_{n=0}^{63} \frac{di_{C,n}}{dt}.$$
(9)

Effects of SSN

• Fluctuation of on-chip V_{DD} and V_{ss} .

$$V_{DD,on-chip} = V_{DD} - v_{L,DD},$$

$$V_{ss,on-chip} = v_{L,ss}.$$
(10)

• Reduce noise margins of digital circuits

 


Figure 15: Reduction of noise margins due to switching noise.

$$NM_{L} = (V_{OH} - V_{L_{dd}}) - V_{IH},$$

$$NM_{H} = V_{IL} - (V_{OL} + V_{L_{ss}}).$$
(11)

Effects of SSN

• Change the Operating Point of Analog Circuits

- \triangleright Consider a MOSFET biased in saturation, the transconductance g_m is given by $g_m = \frac{\partial i_D}{\partial v_{GS}} \approx \frac{2I_D}{V_{GS} V_T}$, where I_D and V_{GS} are channel current and gate-source voltage at dc biasing point. Both I_D and V_{GS} are functions of $V_{DD,on-chip}$.
- ▷ SSN imposes stringent requirements on analog circuits. Analog circuits need to be differentially configured in mixed analog/digital circuits —→ increased circuit complex.

 


Figure 16: Mixed analog/digital circuits.

Effects of SSN (cont'd)

- Change of Operating Point of Analog Circuits (cont'd)
 - ightharpoonup High power noise rejection \longrightarrow difficult to design. If V_{DD} fluctuation is of a critical concern, Fig.17(a) should be used. The head biasing current source behaves as an OPEN-CIRCUIT for V_{DD} switching noise and isolates the circuit from V_{DD} rail.
 - \triangleright If V_{ss} fluctuation is of a critical concern, Fig.17(b) should be used. The tail biasing current source behaves as an OPEN-CIRCUIT for V_{ss} switching noise and isolates the circuit from V_{ss} rail.
 - ▶ Cascodes and regulated cascodes are widely used in realizing these biasing current sources to maximize the resistance of the current sources.

 


Figure 17: Differential configurations.

Effects of SSN (cont'd)

• Increase the Timing Jitter of Oscillators/Clocks


 


Figure 18: Timing jitter due to switching noise.

- \triangleright The threshold crossing points of ring oscillators vary due to the noise (thermal and flicker noise) of the transistors. Such a variation is quantified by $\overline{\Delta \tau}^2$ the timing jitter.
- \triangleright Assume threshold voltage $V_{TH} = V_{DD,on-chip}/2$. For rising edge,

$$V_{DD,on-chip} = v_C + R_p C \frac{dv_C}{dt}, (12)$$

 where R_p is the equivalent channel resistance of pMOS. It is seen that v_C , subsequently, the threshold-crossing point, vary with $V_{DD,on-chip}$, which is a function of switching noise.



- \bullet Simplified Analysis of SSN
- SSN in Sub-micron CMOS Circuits

Simplified Analysis of SSN

• Assumptions

- ▶ Triangle waveform of charging/discharging current.
- $\,\triangleright\,$ Neglect channel resistance of transistors.

 


Figure 19: Simplified analysis of SSN.

Simplified Analysis of SSN (cont'd)

• Analysis

- \triangleright Total charge stored in C_L before discharging $Q = C_L V_{DD}$.
- \triangleright Total charge through L when C_L is completely discharged $Q = \int_0^{t_s} i_L(t) dt = I_{avg} t_s = \frac{I_{max}}{2} t_s$.
- \triangleright Charge conservation : $C_L V_{DD} = \frac{I_{max}}{2} t_s$
- \triangleright Because $\left[\frac{i_L(t)}{dt}\right]_{max} = \frac{I_{max}-0}{t_s/2-0} = \frac{2I_{max}}{t_s}$, we have

$$\left[\frac{di_L}{dt}\right]_{max} = \frac{4C_L V_{DD}}{t_s^2} \tag{13}$$

- \triangleright Example: L=5nH, $t_s=5$ ns, $C_L=10$ pF, $V_{DD}=5$ V, $L\left[\frac{di_L}{dt}\right]_{max}=40$ mV.
- \triangleright SSN is extremely sensitive to t_s . Trade-offs between speed (t_s) and SSN are made in design of output buffers. The speed of output buffers should be set to the lowest possible value to minimize switching noise.

SSN in Sub-micron CMOS Circuits

• Sub-micron MOSFETs

- \triangleright Sub-micron : channel length is less than 1μ m.
- ▶ Sub-micron MOS transistors exhibit velocity saturation due to excessive lateral electric field and mobility degradation due to excessive vertical electric field.

 


Figure 20: Velocity saturation and mobility degradation.

 \triangleright Square-law does not hold for sub-micron MOS transistors. Instead, α -power law applies.

$$i_D = \begin{cases} 0 & \text{if } v_{GS} < V_T \text{ (cutoff)} \\ k_l (v_{GS} - V_T)^{\alpha/2} & \text{if } v_{DS} < v_{DS,sat} \text{ (Triode)} \\ k_s (v_{GS} - V_T)^{\alpha} & \text{if } v_{DS} > v_{DS,sat} \text{ (Saturation)} \end{cases}$$
(14)

where
$$k_l = \mu_n C'_{ox}(W/L)$$
, $k_s = \frac{1}{2}\mu_n C'_{ox}(W/L)$. Typically, $1 < \alpha < 1.2$

• Analysis

 \triangleright For a total of n output drivers that switch simultaneously, the total current

$$i_{DS,total} = ni_{DS} = nk_s(v_{in} - V_T - v_n)^{\alpha}$$
(15)

 \triangleright SSN

$$v_n = L_{ss} \frac{di_{DS,total}}{dt}$$

$$= L_{ss} n k_s \alpha (v_{in} - V_T - v_n)^{\alpha - 1} \frac{d(v_{in} - v_n)}{dt}$$
(16)

 \triangleright Because $a\approx 1$, $(v_{in}-V_T-v_n)^{\alpha-1}\approx 1$ We therefore have

$$v_{n} = L_{ss}nk_{s}\alpha \frac{(dv_{in} - v_{n})}{dt}$$

$$= L_{ss}nk_{s}\alpha \frac{dv_{in}}{dt} - L_{ss}nk_{s}\alpha \frac{dv_{n}}{dt}$$
(17)

This gives

$$\frac{dv_n}{dt} + \frac{v_n}{\alpha n L_{ss} k_s} = \frac{dv_{in}}{dt} \tag{18}$$

▶ Input waveform

 


Figure 21: SSN analysis.

▷ Slopes

Slope of the rising section of the input

$$\frac{dv_{in}}{dt} = S_r = \frac{V_{DD}}{t_r} \tag{19}$$

▶ Equation for the rising section

Substituting the slope (the rising section of the input)

$$\frac{dv_n}{dt} + \frac{v_n}{\alpha n L_{ss} k_s} = S_r, \qquad v_n(t_n) = 0, t_n = \frac{V_T}{S_r}, t_n \le t \le t_r \qquad (20)$$

This is a first-order ODE.

▷ Solution

• Homogeneous ODE - general solution

$$\frac{dv_n}{dt} = -\frac{v_n}{\alpha n L_{ss} k_s} \tag{21}$$

$$v_n = Ae^{-\frac{(t-t_n)}{\alpha n k_s L_{ss}}}, t \ge t_n \tag{22}$$

• Special solution $(v_n = C \text{ (constant)})$

$$\frac{C}{\alpha n k_s L_{ss}} = \frac{V_{DD}}{t_r} \tag{23}$$

which gives

$$C = \frac{V_{DD}}{t_r} n k_s L_{ss} \tag{24}$$

• Complete solution

$$v_n(t) = \frac{V_{DD}}{t_r} \alpha n k_s L_{ss} + A e^{-\frac{(t-t_n)}{\alpha n k_s L_{ss}}}$$
 (25)

• Match the initial condition at $t_n = \frac{V_T}{S_r}, v_n(t_n) = 0$

$$A = -\frac{V_{DD}\alpha n k_s L_{ss}}{t_r} \tag{26}$$

• Complete solution

$$v_n(t) = \frac{V_{DD}\alpha nk_s L_{ss}}{t_r} \left[1 - e^{-\frac{(t-t_n)}{\alpha nk_s L_{ss}}} \right], \quad t_n \le t \le t_r.$$
 (27)

▶ Remarks:

 $\triangleright v_n(t)$ is proportional to

- n (number of switching buffers)
- L_{ss} (bond wire inductance)
- $k_s = \frac{1}{2}\mu_n C'_{ox}(W/L)_n$ (buffer size)
- $1/t_r$ (switching time)

▶ The maximum SSN

$$V_{n,max} = \frac{\alpha V_{DD} n k_s L_{ss}}{t_r} \tag{28}$$

 \triangleright For a reliable operation, $V_{n,max} \le V_T$ is generally required. This yields the limiting condition

$$\frac{\alpha V_{DD} nk L_{ss}}{t_r} = V_T \tag{29}$$

from which n and W can be determined for given V_T and t_r .

SSN Reduction Techniques

• Separate power and ground pins and pads for analog and digital circuits whenever possible

 


Figure 22: Separate analog and digital pins and pads.

▷ Switching noise generated by the digital portion of the system will not affect the operation of the analog portion of the systems.

• Multiple pads and pins for power and ground

 


Figure 23: Multiple pins and pads.

ightharpoonup Increase the number of pins \longrightarrow smaller inductance \longrightarrow lower SSN.

• Multiple pads and pins for power and ground (cont'd)

 


Figure 24: Effect of multiple pins.

 \triangleright Increase the number of pins \longrightarrow better linearity of SSN.

- Avoid using corner pads
 - \triangleright Corner pads have long bonding wires \longrightarrow large self-inductances.
 - ▶ Most design rules require dummy pads (pads with no connection) at corners.
- Use center pads for V_{DD} and $V_{ss} \longrightarrow$ smaller inductance, smaller SSN.
 - ▷ Short bond wires, small self-inductances.

• Pre-driver skewing

- ➤ To prevent the entire buffer (multi-finger layout multiple smaller inverters connected in parallel) to switch at the same time.

 


Figure 25: Multi-finger layout of output buffers. Both drain and source are shared by neighboring fingers.

 


Figure 26: Schematic of the equivalent circuit of output buffers with a multi-finger layout.

• Pre-driver skewing (cont'd)

 


Figure 27: Output buffer with pre-skew.

- $ightharpoonup R_n, R_p = \text{lumped n-well or poly resistors}, C_n, C_p = \text{gate-source capacitance}.$ P_1/N_1 turn on first, P_1/N_1 turn on second, and P_M/N_M turn on the last.
- ▷ Drawback reduced speed. Compromise between SSN and speed must be made.

- Pre-driver skewing (cont'd)
 - ▶ Use Gate Series Resistance for skewing

 


Figure 28: Pre-driver skewing using the gate series resistance.

 \triangleright Less effective for silicide processes because the sheet resistance of gate ploy is small (approximately $7\Omega/\square$).

• On-chip decoupling (bypass) capacitors


 


Figure 29: On-chip decoupling (bypass) capacitors.

- \triangleright On-chip decoupling capacitors are effective in reducing SSN generated by internal logic circuits because they prevent current spikes generated by the internal logic circuits from going to L_{ss} and L_{DD} by providing a local AC path. On-chip decoupling capacitors serve as local charge reservoirs.
- ▷ On-chip decoupling capacitors must be very large in order to be effective, usually comparable to the total area of all transistors on chip (10-20% of total silicon area) very expensive!
- ▷ Resistance is needed to avoid the self resonance formed by the on-chip decoupling capacitors and bond wires — on-chip decoupling capacitors are typically implemented using MOS capacitors. The channel resistance of MOS capacitors are beneficial in minimizing the self resonance of the preceding LC networks.

 

• Hierarchy of decoupling capacitors (cont'd)

 


Figure 30: Hierarchy of on-chip de-coupling capacitors.

- ▶ Both off-chip and on-chip decoupling capacitors are required to minimize switching noise.
- ▶ Decoupling capacitors must be placed as close as possible to hot spots (noise sources) to eliminate generated switching noise locally.
- ➤ Traces and interconnects for decoupling capacitors must have a low impedance at high frequencies such that a low-impedance path exists to eliminate switching noise.

• Fully-balanced buffers

 


Figure 31: Balanced buffers.

 \triangleright Each buffer conveys a fully differential current to the channel. Each buffer draws a constant current from the supply and injects a constant current to the ground. No net rate change of the current flowing through V_{DD} and ground pins - no switching noise.

• Fully-balanced buffers (cont'd)

 


Figure 32: Balanced buffers.

- ▶ In the left figure, low-voltage-differential-signaling (LVDS) is used. The logic state of the output is represented by the direction of the output current. The channel is terminated at the far end by the termination resistor. The resistor also converts the current into a voltage.
- ▶ In the right figure, the channel is terminated with the line characteristic impedance at the near end of the channel.

• Current-mode logic circuits

 \triangleright Use logic circuits that draw a constant current from V_{DD} and inject a constant current to V_{ss} . Current-mode logic (CML) circuits, fully differential logic circuits belong to this category.

 


Figure 33: Current-mode logic gates.

- \triangleright CML circuits draw a constant static current from V_{DD} regardless of its logic states $\longrightarrow C_L \frac{di_L}{dt} = 0$, resulting in zero switching noise.
- ▷ CML circuits consume static power. They are typically used for I/Os or in applications where switching noise is critical.
- \triangleright CML circuits consume less power as compared with static logic circuits at very high frequencies. This is because the dynamic power consumption of static circuits is governed by $P_d = aCfV_{DD}^2$, where a=switching activity parameter, f=frequency. It is evident that P_d is directly proportional to f. The power consumption of CML circuits is independent of f!

Design Criteria for SSN

• SSN must less than Threshold Voltages

 \triangleright For a reliable operation, $V_{n,max} < V_T$ is generally required.

▷ Switching noise derived before

$$v_n(t) = \frac{\alpha V_{DD} n k_s L_{ss}}{t_r} \left[1 - e^{-\frac{(t-t_n)}{\alpha n k_s L_{ss}}} \right], \quad t_n \le t \le t_r.$$
 (30)

This yields

$$\frac{\alpha V_{DD} n k L_{ss}}{t_r} = V_T, \tag{31}$$

from which n and W can be determined for given V_T , f, and t_r .

Analog and Digital Grounding

• Substrate Modeling

- ▶ Resistive paths exist from p+ contacts to p-substrate. A voltage change of p+ contacts affects the voltage of substrate.
- ▷ Capacitive paths exist from p+/n-well, n+/p-substrate, and n-well/p-substrate junctions.

 


Figure 34: Lumped models of heavily doped substrates.

 $ightharpoonup R_{12}\gg R_{11}, R_{22}$. $R_{12}=$ resistance between contacts, $R_{11},$ $R_{22}=$ resistance from contacts to the backplane. Most of substrate noise will travel vertically down to the backplane. The backplane must be grounded properly to avoid the distribution of substrate noise to the entire chip. (Ref.: B. Owens et al. "Simulation and measurement of supply and substrate noise in mixed-signal ICs," *IEEE J. Solid-State Circuits*, Vol.40, No.2, pp. 382-391, Feb. 2005).

• Separate analog and digital power pads and bonding wires for analog and digital circuits.

 


Figure 35: Separate analog and digital V_{DD} pads and bonding wires for analog and digital circuits.

 \triangleright Digital V_{DD} rails are much more noisy as compared with analog V_{DD} .

• Separate analog and digital ground pads and bonding wires for analog and digital circuits.

 


Figure 36: Separate analog and digital V_{ss} pads and bonding wires for analog and digital circuits.

 \triangleright Digital V_{ss} rails are much more noisy as compared with analog V_{ss} .

• Separate analog and digital substrate connections.

 


Figure 37: Separate analog and digital substrate connections.

- ▶ Analog substrates are typically protected by guard rings. They are less noisy as compared with digital substrates.
- \triangleright Connecting analog substrate to the outside ground directly can lower the voltage fluctuation of the analog substrate. Downside: body effect occurs as $V_T = V_{To} + \gamma \left(\sqrt{V_{sb} + |2\phi_F|} \right) \sqrt{|2\phi_F|}$, where γ is body-effect coefficient and $\phi_F \approx 0.6 \text{V}$ is the Fermi potential.
- ▶ If analog substrates are well protected, then the source of MOSFETs and analog substrates can be tied together to eliminate the body effect. Example differential pairs.

 


Figure 38: Differential configuration.

- \triangleright Single-ended configuration v_{GS} is directly affected by ground bouncing.
- ▶ The output of differential-mode configurations is insensitive of SSN as the biasing circuitry provides a constant biasing current to the differential pair regardless of ground bouncing.
- ▷ Deep sub-micron MOS transistors have a small output impedance, reducing the effectiveness of the biasing circuitry. Cascode is generally mandatory in biasing circuits to minimize the effect of ground bounding.

• Passive Guard-Rings

- ▶ Use passive guard-rings to isolate sensitive circuits from noisy digital circuits.
- ⊳ p+ guard rings p+ diffusion contacts on p-substrate to collect holes. n+ guard rings - n+ diffusion contacts in n-wells to collect electrons.
- ▷ Guard ring resistance should be made as low as possible → guard rings should be made as wide as possible.
- ▷ Guard rings should be placed as close as possible to noise sources.

 


Figure 39: p-type passive guard rings.

• Active Guard Rings

 


Figure 40: Active passive guard rings (Ref. K. Fukuda et al., "Substrate noise reduction using active grant band filters in mixed-signal integrated circuits," *IEICE Trans. Fundamentals of Electronics, Communications and Computer Sciences*, Vol. E80-A, pp.313-320, Feb. 1997).

- ▶ Use active guard-rings to ACTIVELY isolate sensitive circuits from noisy digital circuits. Active guard rings perform better as compared with passive guard rings.
- \triangleright The inverting voltage buffer must have a large bandwidth in order to be effective in suppressing substrate noise. This is because v_n contains a significantly large number of high-frequency components and these components must appear at the output of the buffer in order to suppress substrate noise.